

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE303 Electronics II

Quiz # 2

Name:	I.D#	No.	Sec.# 02
-------	------	-----	----------

For the circuit shown below, assume the opamp has an input resistance r_i , output resistance r_o , and open load gain of ∞ .

- (a) What type of feedback topology is applied?
- (b) Draw complete circuit A of the given feedback network.

