

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE-303 Electronics II
Exam I (042)

Name:	I.D#	No.	Sec.#
-------	------	-----	-------

Q1) The amplifier in Fig. 1 is biased to operate at $I_D=1\text{mA}$ and $g_m=1\text{mA/V}$. Neglecting r_o , Find the high frequency poles if $C_{gs}=1\text{pF}$ and $C_{gd}=0.2\text{pF}$ [40 Marks]

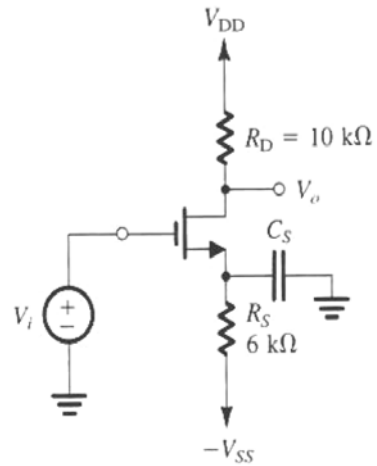


Fig. 1

Q2) For the common-emitter amplifier of Fig. 2, neglect r_x and r_o , and assume the current source ideal. Assume $I=1\text{mA}$, $R_{\text{sig}}=R_C=R_L=10\text{k}\Omega$,

(a) Derive expressions for high frequency pole(s) due to the BJT internal capacitances

(b) Find the dominant high frequency pole value assuming $f_T=600\text{MHz}$, $C_\mu=2\text{pF}$, and $\beta_0=100$.

(Hint: $f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$)

(c) Select the values of C_E and C_C such that the dominant low frequency pole will be at 100Hz while minimizing the total capacitance. [50Marks]

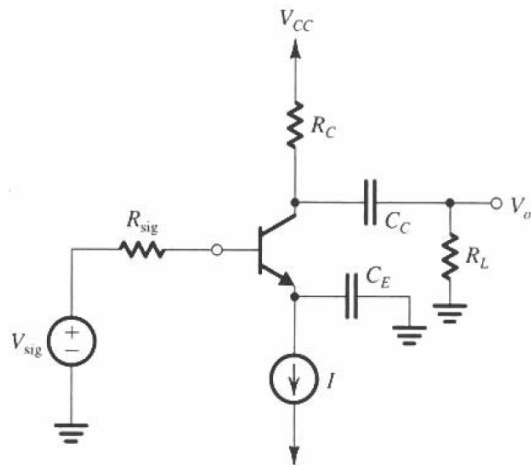


Fig. 2

Q3) (a) Investigate the effect of the biasing and offset currents of the op-amp on the performance of the inverting integrator.

(b) A non-inverting amplifier employs an op amp having a dc gain of 10^4 and unity-gain frequency of 10^6 Hz. What is the amplifier bandwidth if it is designed with a gain of 25V/V. [60Marks]