

**King Fahd University of Petroleum and Minerals**  
**Electrical Engineering Department**  
**EE303 Electronics II**

**Exam # II**

Name:	I.D#	No.	Sec.#
-------	------	-----	-------

**5/15**

**Question No.1**

Assume the op amp is ideal.

- (a) Drive the voltage transfer function for the bandpass filter shown in Fig. 1.
- (b) If  $R_1=10k\Omega$ , design the filter such that the magnitude of the midband gain is 50 and the 3dB cutoff frequencies are 200Hz and 5kHz.


**Fig. 1**

**Question No.2**

Consider the amplifier in Fig. 2. The op-amp parameters are  $A_v=5000$ ,  $R_i=1\text{k}\Omega$ , and  $R_o=1\text{k}\Omega$ , and the transistor parameters has  $\beta_o=100$  and biased to have  $g_m=8\text{mA/V}$  and  $r_o=100\text{k}\Omega$ .

(a) Which type of feedback topology is incorporated?

(b) Use feedback analysis to find values for closed loop gain  $v_o/v_i$  and input and output resistances.

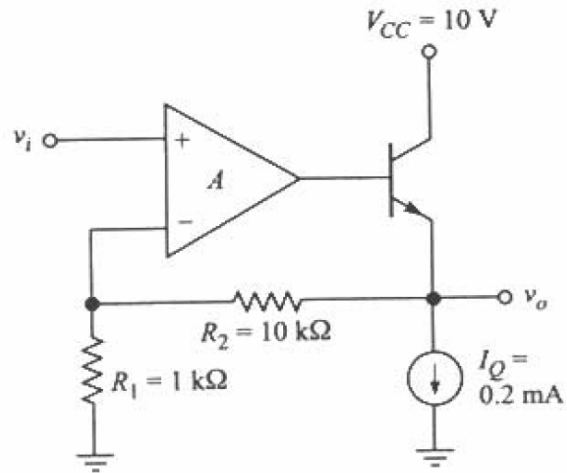


**Fig. 2**

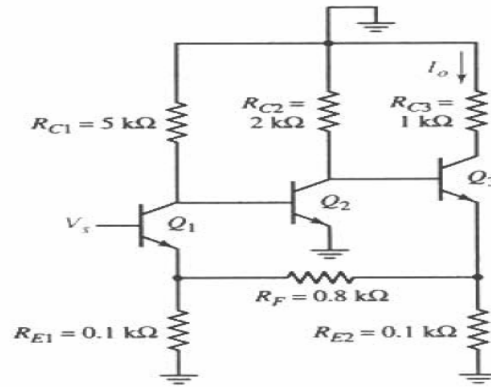
**Question No.3**

(a) Determine the type of feedback and calculate the feedback factor  $\beta$  for each amplifier shown in Fig. 3.


(b) Find approximate value for the transconductance gain  $\frac{I_o}{V_s}$  for the amplifier shown in Fig. 3(b).



(a)

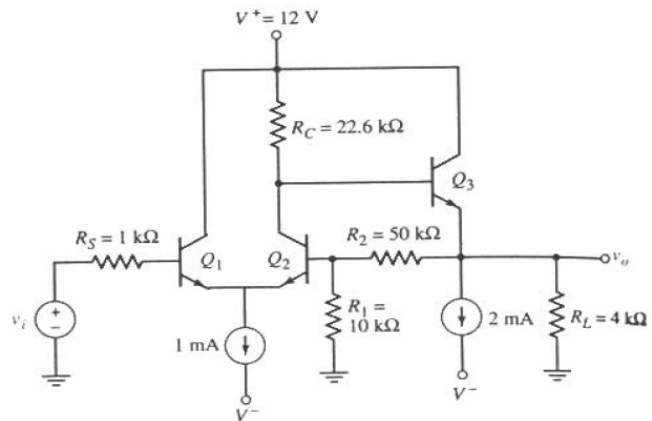

(b)

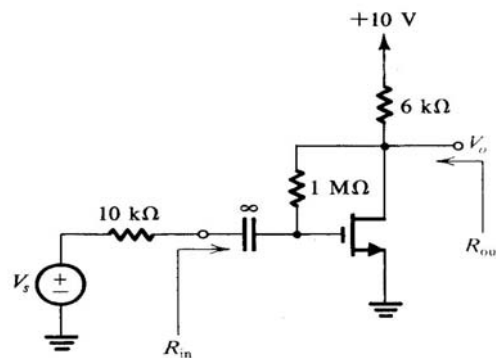

(c)

**Fig. 3**