

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE303 Electronics II

Quiz # 2

| | | | |
|-------|------|-----|----------|
| Name: | I.D# | No. | Sec.# 01 |
|-------|------|-----|----------|

Assume the op-amp exhibits a finite open-loop gain (A). Find the transfer function of the op-amp based inverting integrator.