

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE303 Electronics II

Quiz # 3

Name:	I.D#	No.	Sec.# 02
-------	------	-----	----------

Assuming an ideal op amp. Drive the transfer function for the second-order low pass filter shown below.

