

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE303 Electronics II

Quiz # 4

| | | | |
|-------|------|-----|----------|
| Name: | I.D# | No. | Sec.# 02 |
|-------|------|-----|----------|

What type of feedback topology is applied?

