

**King Fahd University of Petroleum and Minerals**  
**Electrical Engineering Department**  
**EE303 Electronics II**

**Quiz # 4**

Name:	I.D#	No.	Sec.# 02
-------	------	-----	----------

What type of feedback topology is applied?

