

EE 203 Electronics I

Quiz # 2

Name:

I.D.#

Sec.# 08

Consider the circuits shown, calculate all the node voltages and branch currents. (i.e V_B , V_C , V_E , I_B , I_C , and I_E) using $\beta = 100$. You need to check any assumption.

