

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS

Electrical Engineering Department

EE-416 Analog Filter Design

Instructor: Dr. Hussain Alzahr

H.W.#1

Due Wednesday, Oct.9, 2005

1. Figure 1 shows an RCL circuit in which  $R_2=1$  and  $L_1$  and  $C_2$  are to be determined so that  $V_2/V_1$  gives a Butterworth frequency response.

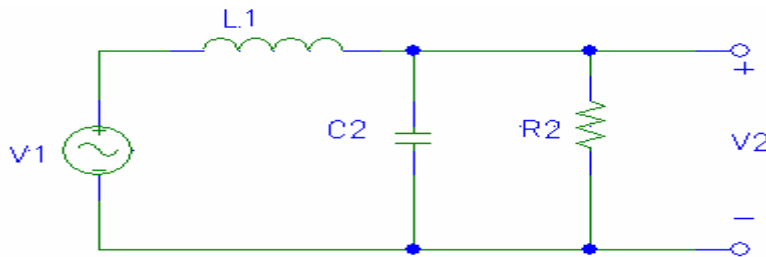


Figure 1

2. A maximally flat magnitude transfer function is characterized by the parameter  $\epsilon = 0.075$  and  $n=7$ . Determine the minimum attenuation at the stopband frequency  $\omega_s = 1.85\omega_p$ . Assume  $f_p = 980$  Hz. Find the transfer function and its poles:

(a) Relying on calculations (b) Relying on Butterworth tables.

3. Consider the following three sets of specifications:

	$\alpha_{\max}$ dB	$\alpha_{\min}$ dB	$\omega_p$ rad/s	$\omega_s$ rad/s
(a)	0.25	15	10,000	14,000
(b)	0.50	30	750	1,750
(c)	1.00	25	1,250	4,375

For each of the three cases do the following:

- (i) Determine  $n$ , the required order of the LP filter with maximally flat magnitude.
- (ii) Determine the actual attenuation at the edge of the passband and the edge of the stop band,  $\alpha(\omega_p)$  and  $\alpha(\omega_s)$ .
- (iii) Determine the attenuation at the frequencies  $2 \times \omega_s$  and  $10 \times \omega_s$ .

4) Design a lowpass filter with a Chebyshev response satisfying the following specifications:  $\alpha_{\max} = 0.25$  dB,  $\alpha_{\min} = 18$  dB,  $\omega_p = 1000$  rad/s,  $\omega_s = 1400$  rad/s. Adjust the gain so the minimum value of  $\alpha(\omega)$  is 0 dB. Magnitude scale so that the element values in your circuit realization are in practical range (Figure 2).

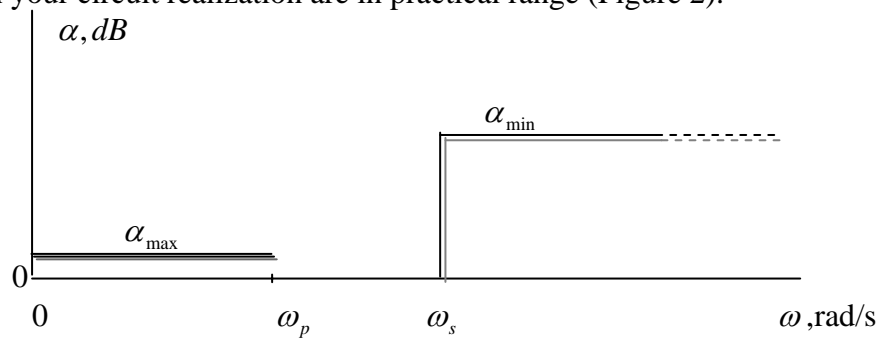


Figure 2

5) Design a lowpass filter with equal ripple passband for the following specifications:

(a) Stopband:  $\alpha_{\min} = 65$  dB at  $f_s = 10.4$  kHz

(b) Passband:  $\alpha_{\max} = 0.5$  dB,  $f_c = 4.5$  kHz

Be sure to scale the frequency variable.

6) For  $\alpha_{\max} = 1$  dB and  $\omega_p = 1$  rad/s find the poles of 12<sup>th</sup>-order lowpass filters based on (a) Butterworth's approximation (b) Chebyshev's Approximation