

EE 203 Electronics I

Quiz # 3

Name:

I.D.#

No.

Sec.# 03

Replace the transistor with its hybrid- π model and draw the amplifier small signal equivalent circuit?

