

**King Fahd University of Petroleum and Minerals**  
**Electrical Engineering Department**  
EE201 Electric Circuits  
**Quiz # 2**

|       |      |          |
|-------|------|----------|
| Name: | I.D# | Sec.# 01 |
|-------|------|----------|

Use nodal analysis (Nodal voltage method) to determine  $V_o$  in the circuit shown.

