

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE201 Electric Circuits

Quiz # 3

Name:	I.D#	Serial #	Sec.# 01
-------	------	----------	----------

The variable resistor in the circuit shown is adjusted for maximum power transfer to R_o :

- a) Find the value of R_o
- b) Find the maximum power that can be delivered to R_o .

