

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE201 Electric Circuits

Quiz # 4

Name:	I.D#	Serial #	Sec.# 01
-------	------	----------	----------

The switch in the circuit shown has been closed a long time. At time $t=0$ it is opened, in position **a** for long time before moving to position **b** at $t=0$.

(a) Find $i_o(t)$ for $t \geq 0$

∴d

