

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE201 Electric Circuits

Quiz # 5

Name:	I.D#	Serial #	Sec.# 02
-------	------	----------	----------

For the circuit shown below, use **Nodal Analysis** to find the Node Voltages \bar{V}_1 & \bar{V}_2 .

