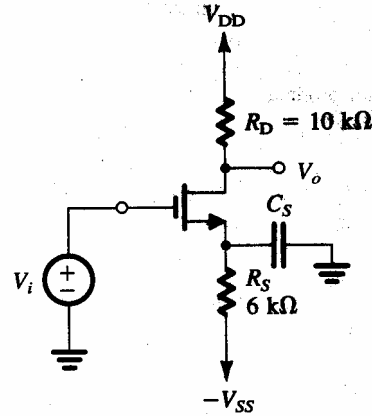


King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE-303 Electronics II
Exam I (061)

Name:	I.D#	No.	Sec.# 01
-------	------	-----	----------

Q1) The amplifier shown is biased such that $g_m=1\text{mA/V}$. Find the value of high frequency poles with and without C_S . Neglect r_o and assume $C_{gs}=0.3\text{pF}$ and $C_{gd}=0.1\text{pF}$.




Q2) For the emitter follower shown below assume $\beta_o = 200$ and neglect r_o and r_x .

(a) Determine the value of the low frequency poles assuming $C_1=C_2=1\mu\text{F}$.

(b) What are frequencies of the low frequency zeroes.

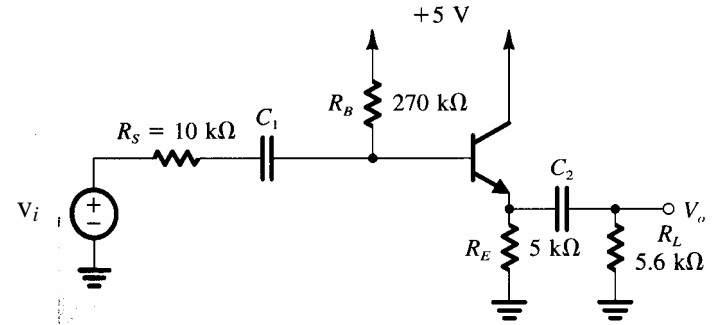(c) Is the bandwidth of this amplifier is expected to be high or low? Why?



- Q3** (a) What is the main problem with the inverting-integrator based on op-amp?
- (b) A non-inverting amplifier with nominal gain of 100V/V employs an op amp having a dc gain of 10^4 and unity-gain frequency of 10^6 Hz. What is the 3dB pole of amplifier? What will be the gain of the amplifier at frequency 10 times the pole?