

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE303 Electronics II

Quiz # 1

Name:	I.D#	No.	Sec.# 01
-------	------	-----	----------

For the common-emitter amplifier shown, neglect r_x and r_o , and assume the current source is ideal.

Find expressions for the **high** frequency poles.

