

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE303 Electronics II

Quiz # 2

Name:	I.D#	No.	Sec.# 01
-------	------	-----	----------

- (a) Design a non-inverting amplifier using an ideal op-amp to provide voltage gain of 100.
- (b) Connect to the amplifier of part (a) two resistors such that the gain would not change. Explain your answer.