

Chp.3: 3, 4, 9, 93, 97, 99, 100, 103 + Redo problems 3, 4, and 9 assuming 0.7V model.