

EE 203 Electronics I  
Quiz # 1

Name: \_\_\_\_\_

I.D.# \_\_\_\_\_

Sec.# \_\_\_\_\_

- Q. Using constant voltage drop model find  $I_{D1}$  and  $V_o$  when  $R_1 = 5k$ ,  $R_2 = 10k$ .  
Indicate the direction of current on the diodes.

