

EE 203 Electronics I
Quiz # 2

Name: _____ **I.D.#** _____ **Ser.#** _____ **Sec.#** _____

For the MOS circuit shown in the figure, $\lambda=0$, $|V_t|=1$ V, and $\mu C_{ox}(W/L) = 1$ mA/V².