

EE 203 Electronics I
Quiz # 5

Name: _____ **I.D.#** _____ **Ser.#** _____ **Sec.#** _____

For the amplifier shown below, the transistor has $\beta=100$ (Do not neglect the base current). Perform DC analysis to find I_C and confirm that the transistors are working in active mode.

