

King Fahd University of Petroleum and Minerals
Electrical Engineering Department

EE201 Electric Circuits

Quiz # 2

Name:	I.D#	Sec.# 0
-------	------	---------

Use nodal analysis (Nodal voltage method) to determine i in the circuit shown.

