

King Fahd University of Petroleum and Minerals
Electrical Engineering Department

EE201 Electric Circuits

Quiz # 3

Name:	I.D#	Sec.#
-------	------	-------

Use mesh analysis to determine i_{Δ} in the circuit shown.

