

King Fahd University of Petroleum and Minerals
Electrical Engineering Department

EE201 Electric Circuits

Quiz # 6

Name:	I.D.#	Sec.# 02
-------	-------	----------

At $t = 0$, the switch in the circuit shown moves instantaneously from position a to position b.

a) Calculate v_o for $t \geq 0^+$.

