

King Fahd University of Petroleum and Minerals
Electrical Engineering Department

EE201 Electric Circuits

Quiz # 5

Name: _____ I.D# _____ Sec.# 03

For the parallel RLC circuit shown below, find $i_C(t)$.

