

# King Fahd University of Petroleum and Minerals


## Electrical Engineering Department

### EE203 Electronics I Exam # 1

Name:	I.D#	No.	Sec.#01
-------	------	-----	---------


#### Question No.1

(a) For the circuit shown in Fig. 1(a), what is the minimum value of  $v_I$  that makes the diode conducting. Use 0.7V constant voltage drop model.

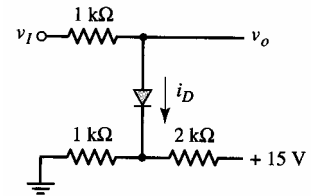

**Fig. 1(a)**

(b) For the circuit shown in Fig. 1(b), explain the operation of the circuit for different values of  $v_I$ . Then, draw the voltage transfer characteristics of the circuit for the range of  $v_I$  from -10V to 10V.

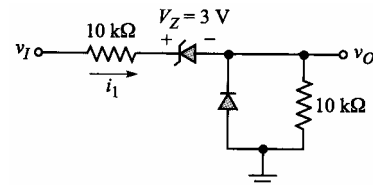


**Fig.1 (b)**

**Question No. 2**

Fig. 2 shows a rectifier using center-tap transformer. Assume that the diode needs 0.7V to conduct and the sinusoidal input signal has amplitude of 110V and frequency of 60Hz.

- (a) Is this a full-wave or half-wave rectifier.
- (b) Calculate the ripple and DC values at the output terminal TP1.
- (c) Sketch the output waveform at TP1.
- (d) If it were required to reduce the ripple further, what circuit would you use?
  - i) a limiter    ii) a regulator    iii) a clipper    iv) an amplifier

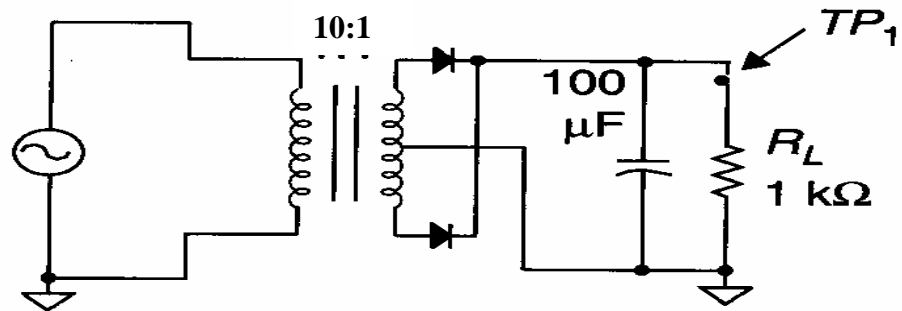

**Fig. 2**

**Question No. 3**

(a) The PMOS in the circuit of Fig. 3(a) has  $V_t = -0.7$  V,  $\mu C_{ox} = 60$   $\mu\text{A}/\text{V}^2$ ,  $L = 0.8$   $\mu\text{m}$  and  $W = 4.8$   $\mu\text{m}$ , and  $\lambda = 0$ . If  $R = 30.4$   $\text{k}\Omega$ , find the drain current and voltage.

(b) The NMOS transistors in Fig. 3(b) have  $V_t = -0.7$  V,  $\mu C_{ox} = 120$   $\mu\text{A}/\text{V}^2$ ,  $L_1 = L_2 = 1$   $\mu\text{m}$ , find the values of the gate width for each of Q1 and Q2 and the value of R, to obtain the current values indicated.