

**King Fahd University of Petroleum and Minerals**  
**Electrical Engineering Department**

**EE203 Electronics I**  
**Exam # II**


Name:	I.D#	No.	Sec.#
-------	------	-----	-------

**Show all your work.**

**Question No.1 [6/15]**

For the circuit in Figure 1, the transistor has  $\beta=100$  and  $R_C=4k\Omega$ .

- (i) Select  $R_E$  such that  $I_C=1\text{mA}$ .
- (ii) Confirm that the transistor is working in active mode.
- (iii) Find the small signal voltage gain  $A_V=v_o/v_s$
- (iv) Determine the input resistance seen by the signal source  $v_s$ .

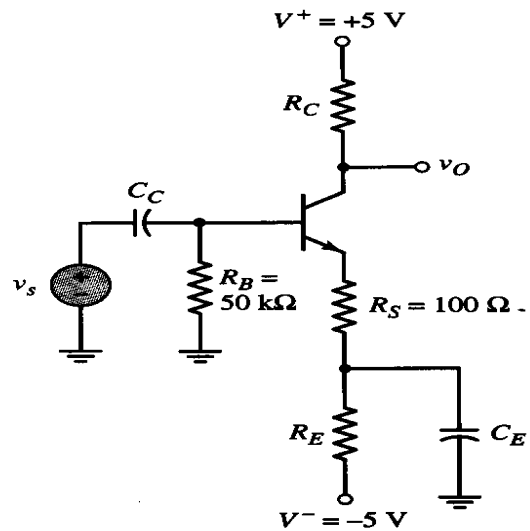


**Figure 1**

**Question No. 2 [6/15]**

Consider the MOSFET amplifier circuit shown, assume  $R_s=10k\Omega$ ,  $\lambda=0$ ,  $V_t= 1V$  and  $\mu C_{ox}W/L=6mA/V^2$ .

- i) Find  $I_D$
- ii) **Confirm** that the transistor working in pinch off.
- iii) Calculate the voltage gain.
- iv) Determine the input and output resistances.

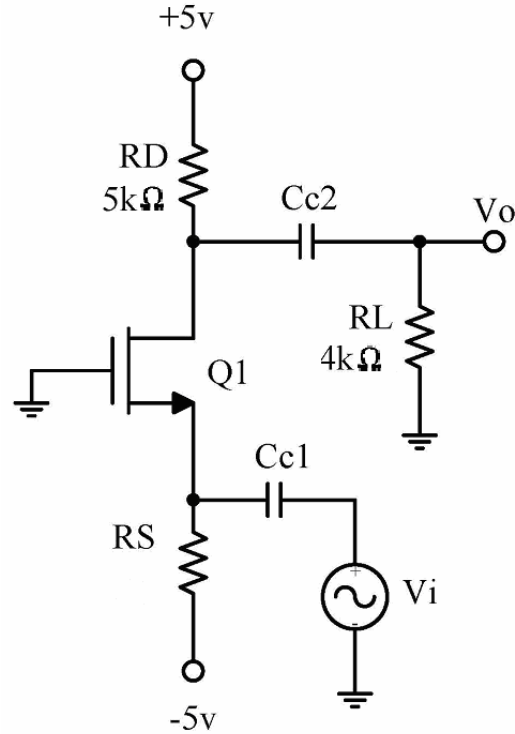


**Figure 2**

**Question No. 3 [3/15]**

Assume that  $\beta = 50$  for the circuit in Fig. 3,

- (a) Show that the BJT is **not** working in active region.
- (b) Suggest how you can redesign the circuit to work in active region. Verify your answer.

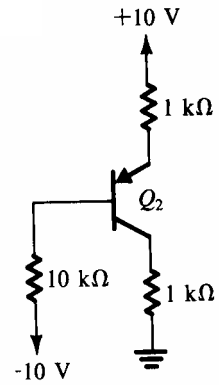

**Fig.3**