

EE 203 Electronics I
Quiz # 4

Name: _____

I.D.# _____

Sec.# _____

For the circuit shown below, find the node voltage V_g . Assume $\mu C_{ox}(W/L) = 0.5\text{mA/V}^2$, $V_t = 2\text{V}$, and $\lambda = 0$.

