

EE 203 Electronics I
Quiz # 4

Name: _____

I.D.# _____

Sec.# 01 _____

For the circuit shown, the transistor has $\beta=100$. Perform DC analysis to find I_C and confirm that the transistor is working in active mode. Then, draw the small signal equivalent circuit.

