

**EE 203 Electronics I**  
**Quiz # 6**

**Name:** \_\_\_\_\_

**I.D.#** \_\_\_\_\_

**Sec.# 01** \_\_\_\_\_

---

Using minimum transistors, design a CMOS logic circuit to implement the function:

$$Y = A.(B + C.D) + E .$$