


Ministry of Higher Education King Fahd University of Petroleum & Minerals Electrical Engineering Department		وزارة التعليم العالي جامعة الملك فهد للبترول والمعادن قسم الهندسة الكهربائية
--	---	---

Major Exam # 1

Electronics I EE 203

Name	
ID#	


Dr. Hussain Al-Zaher	Dr. Adnan Andulasi	Dr. Munir Al-Absi

Problem #1	
Problem # 2	
Problem # 3	
Total Grade	

Problem # 1 (10) points

Assume that diodes need 0.7V to conduct.

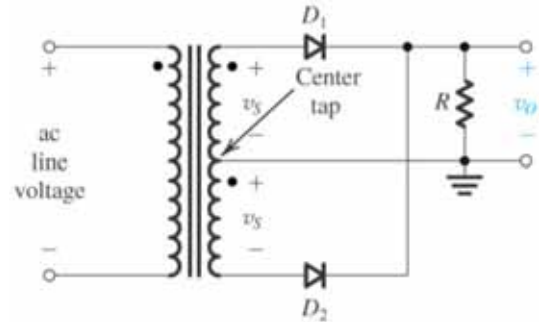- (a) For the rectifier shown below, if V_s is sinusoidal with amplitude of 15V and frequency of 60Hz. Calculate the peak inverse voltage (PIV). [2 points]
- (b) If smoothing capacitor is added in parallel with R, design the rectifier to produce an output DC voltage of 12V with a ripple of not more than 0.6V. Assume an ac line voltage of 110V (rms) and 60Hz is available. [5points]
- (c) Suggest two ways to further reduce the ripple. [3 points]




Problem # 2

(a) 5 points

Consider the diode circuit below.

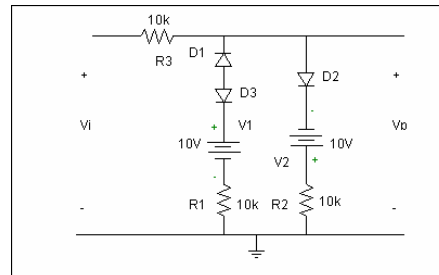
- 1) State what type application can this circuit be used for (i.e., rectifier, limiter, etc)?
[1 point]
- 2) Assume a constant voltage drop model for the diodes ($V_D=0.7V$). Derive and sketch the transfer characteristic function of the circuit (V_O as a function of V_I). Assume V_I can vary from -20 to 20 Volt. **[4 points]**



Problem # 2

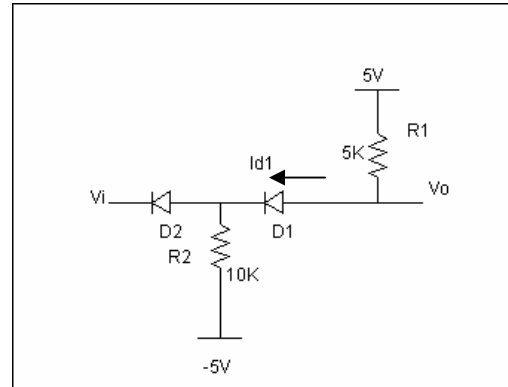Part b (5 Points)

In the circuit shown, if $V_i = 0$, determine the output voltage V_o and the diode current I_{D1} . Assume $V_{DOn} = 0.7V$



Problem # 3(10 points)

For the nMOS circuit shown, answer the following questions

If $V_S = 0$

(a) What is the mode of operation of the transistor? Justify your answer [2point]

(b) Find the drain current, assume $K_n' \frac{W}{L} = 1mA$ and the threshold voltage $V_{TH} = 1V$

[5points]

(c) Find the gate voltage V_{GS} [1 point]

If $V_S = 5V$

(d) Find the drain current I_d and the drain Voltage V_d [2 points]

