

EE 203 Electronics I

Quiz # 1


Name: _____

I.D.# _____

No. _____

Sec.#02 _____

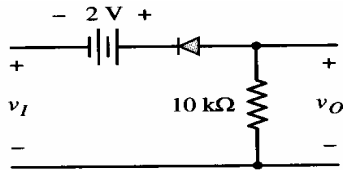Referring to the circuit shown below, complete the table assuming constant voltage drop model for forward biased diodes ($0.7V$).



v_I	v_o
-10V	
-4V	
0	
4	
10	