

# EE 203 Electronics I

## Quiz # 4

Name:

I.D.#

No.

Sec.#

---

Draw the BJT amplifier small signal equivalent circuit. Assuming  $g_m=40\text{mA/V}$  and  $r_\pi=0.625\text{k}$ , calculate the voltage gain.

