

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
Electrical Engineering Department
EE-416 Analog Filter Design
Instructor: Dr. Hussain Alzaher
Exam-I (071)

Name:

I.D.#

Serial #:

1) Use an ideal op-amp for designing a circuit to realize the bilinear transfer function with a pole at 1 kHz and a zero at 10 kHz, and high-frequency gain of 20 dB. **Show your final design.**

2) Design a Sallen-Key lowpass biquad using an ideal-opamp to realize Butterworth response with gain 0 dB, $Q = 0.707$, and $f_o = 100\text{kHz}$. **Show your final design.**

3) Design a Delyiannis-Friend bandpass circuit with $Q = 10$, and $f_o = 100\text{kHz}$ and $H_M = 10\text{dB}$. **Show your final design.**

(4) Determine the non-ideal effects in the parameters and responses of the filters designed in problems (1), (2) and (3), when they are realized using real op-amps with $\omega_t = 2\pi 100$ Mrad/sec.