

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
Electrical Engineering Department
EE-416 Analog Filter Design
Instructor: Dr. Hussain Alzaher
Quiz.#3

Name: _____

I.D.# _____

Serial #: _____

3) For the circuit given in Figure below, find the voltage transfer function $T(s)$.
Briefly explain what would be the main differences between the ideal and practical responses.

