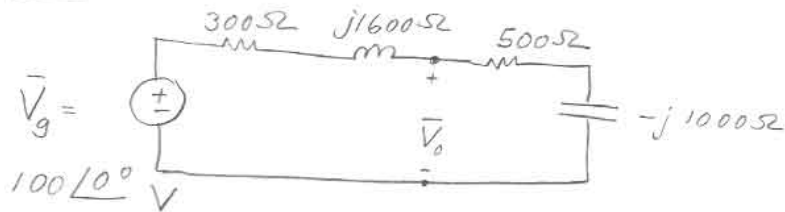


## EE201 HW#12

(1)


9.36

$$\begin{aligned} \bar{V}_o &= \frac{(500 - j1000)}{(500 - j1000) + (300 + j1600)} \times 100 \angle 0^\circ \\ &= \frac{(1118.0 \angle -63.435^\circ)(100 \angle 0^\circ)}{800 + j600} \\ &= \frac{1.118 \times 10^5 \angle -63.435^\circ}{10^3 \angle 36.87^\circ} = 111.8 \angle -100.31^\circ \end{aligned}$$

$$\therefore v_o(t) = 111.8 \cos(8000t - 100.31^\circ) \text{ V}$$

9.38

(2)

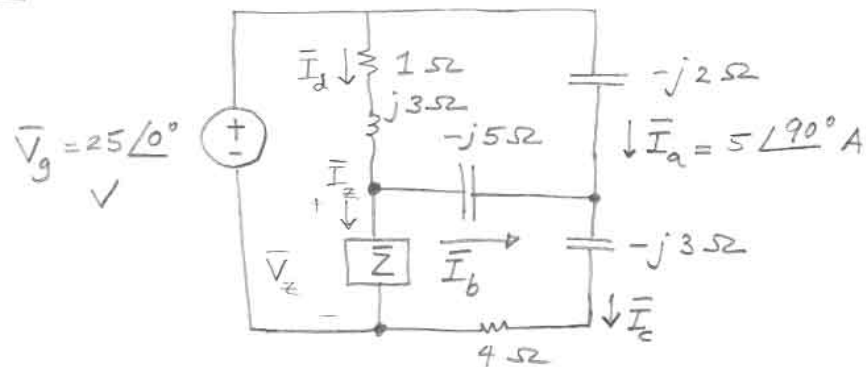

$$\text{KVL} \Rightarrow -V_g + (-j2) \bar{I}_a + (-j3+4) \bar{I}_c = 0$$

$$-25 + (-j2)(j5) + (4-j3) \bar{I}_c = 0$$

$$\bar{I}_c = \frac{15}{4-j3} = \frac{15}{5 \angle -36.87^\circ} = 3 \angle 36.87^\circ \text{ A}$$

$$= (2.4 + j1.8) \text{ A}$$

$$\bar{I}_b = \bar{I}_c - \bar{I}_a = (2.4 + j1.8) - j5 = 2.4 - j3.2 \text{ A}$$

$$\bar{V}_z = (-j5) \bar{I}_b + (4-j3) \bar{I}_c$$

$$= (-j5)(2.4 - j3.2) + (4-j3)(2.4 + j1.8)$$

$$= -1 - j12 \text{ V}$$

$$-25 + (1+j3) \bar{I}_d + \bar{V}_z = 0 \Rightarrow$$

$$-25 + (1+j3) \bar{I}_d + (-1-j12) = 0$$

$$\therefore \bar{I}_d = \frac{26 + j12}{1 + j3} = 6.2 - j6.6 \text{ A}$$


Ⓒ

$$\begin{aligned}\bar{I}_z &= \bar{I}_d - \bar{I}_b = (6.2 - j6.6) - (2.4 - j3.2) \\ &= 3.8 - j3.4 \text{ A}\end{aligned}$$

$$\therefore \bar{Z} = \frac{\bar{V}_z}{\bar{I}_z} = \frac{-1 - j12}{3.8 - j3.4} = 1.42 - j1.88 \Omega$$

9.42

(4)


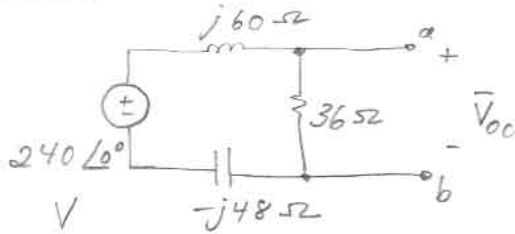


$$\begin{aligned}\bar{V}_{oc} &= \frac{36}{j60 + 36 - j48} \times 240 \angle 0^\circ \\ &= \frac{36(240 \angle 0^\circ)}{36 + j12} = \frac{8640 \angle 0^\circ}{37.947 \angle 18.435^\circ} \\ &= 227.69 \angle -18.435^\circ = \bar{V}_{th}\end{aligned}$$

$$\begin{aligned}\bar{Z}_{th} &= 36 \parallel (j12) = \frac{36(j12 \angle 90^\circ)}{36 + j12} \\ &= \frac{432 \angle 90^\circ}{37.947 \angle 18.435^\circ} \\ &= 11.38 \angle 71.565^\circ = 3.599 + j10.796 \\ &\quad \Omega\end{aligned}$$

9.53

(5)

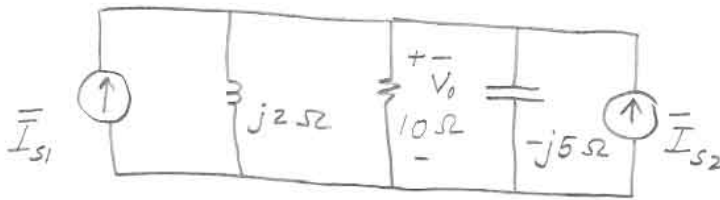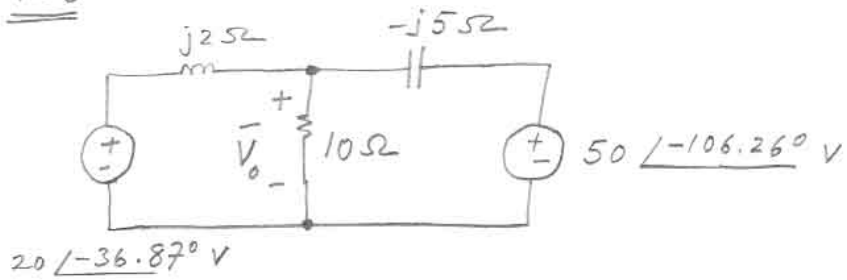

$$\bar{I}_{s1} = \frac{20 \angle -36.87^\circ}{j2} = 10 \angle -126.87^\circ$$


$$\bar{I}_{s2} = \frac{50 \angle -106.26^\circ}{-j5} = 10 \angle -16.26^\circ$$

$$\begin{aligned}\bar{Y} &= \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 = \frac{1}{j2} + \frac{1}{10} + \frac{1}{-j5} \\ &= -j0.5 + 0.1 + j0.2 = 0.1 - j0.3\end{aligned}$$

$$\therefore \bar{Z} = \frac{1}{0.1 - j0.3} = 1 + j3 \Omega$$

$$\begin{aligned}\bar{I}_{tot} &= \bar{I}_{s1} + \bar{I}_{s2} = 10 \angle -126.87^\circ + 10 \angle -16.26^\circ \\ &= (-6 - j8) + (9.6 - j2.8) = 3.6 - j10.8 \text{ A}\end{aligned}$$

6

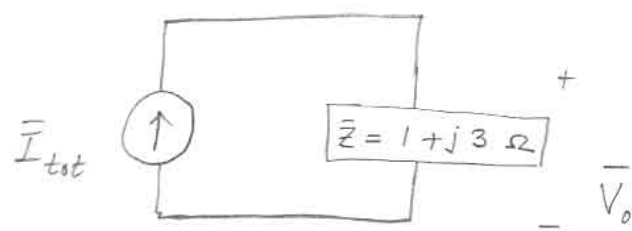

$$= 3.6 - j10.8 \text{ A}$$

$$\begin{aligned}\bar{V}_o &= \bar{I}_{tot} \bar{Z} = (3.6 - j10.8)(1 + j3) \\ &= (11.384 \angle -71.565^\circ)(3.162 \angle 71.565^\circ) \\ &= 36 \angle 0^\circ\end{aligned}$$

$$\therefore v_o(t) = 36 \cos(2000t) \text{ V}$$