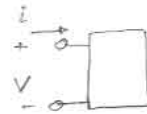


10.1

$$a) \bar{V} = 100 \angle 50^\circ \text{ V}, \bar{I} = 10 \angle 15^\circ \text{ A}$$



$$P = \frac{1}{2} IV \cos \theta = \frac{1}{2} (10)(100) \cos(50^\circ - 15^\circ) = 409.58 \text{ W}$$

$$Q = \frac{1}{2} IV \sin \theta = \frac{1}{2} (10)(100) \sin(50^\circ - 15^\circ) = 286.79 \text{ VAR}$$

The circuit absorbs 409.58 W and absorbs 286.79 VAR.

$$b) \bar{V} = 40 \angle -15^\circ \text{ V}, \bar{I} = 20 \angle 60^\circ \text{ A} \Rightarrow \theta = -15^\circ - 60^\circ = -75^\circ$$

$$P = \frac{1}{2} (20)(40) \cos(-75^\circ) = 103.53 \text{ W (abs.)}$$

$$Q = \frac{1}{2} (20)(40) \sin(-75^\circ) = -386.37 \text{ VAR (del.)}$$

$$c) \bar{V} = 400 \angle 30^\circ \text{ V}, \bar{I} = 10 \angle 150^\circ \text{ A}$$

$$\therefore \theta = -120^\circ$$

$$P = \frac{1}{2} (10)(400) \cos(-120^\circ) = -1000 \text{ W (del.)}$$

$$Q = \frac{1}{2} (10)(400) \sin(-120^\circ) = -1732.05 \text{ VAR (del.)}$$

$$d) \bar{V} = 200 \angle 160^\circ \text{ V}, \bar{I} = 5 \angle 40^\circ \text{ A}$$

$$\therefore \theta = 120^\circ$$

$$P = \frac{1}{2} (5)(200) \cos(120^\circ) = -250 \text{ W (del.)}$$

$$Q = \frac{1}{2} (5)(200) \sin(120^\circ) = 433.01 \text{ VAR (abs.)}$$

10.7

$$I_{rms} = \sqrt{\frac{\text{Area under the square}}{\text{Period}}} = \sqrt{\frac{\int_{t_0}^{t_0+T} i^2(t) dt}{T}} \quad (2)$$

$$T = 0.1 \text{ s}$$

$$i(t) = \begin{cases} 200t & , 0 \leq t \leq 0.075 \text{ Sec} \\ 60 - 600t & , 0.075 \leq t \leq 0.1 \text{ Sec} \end{cases}$$


$$\text{Let } t_0 = 0.$$

$$\begin{aligned} \therefore \int_0^{0.1} i^2(t) dt &= \int_0^{0.075} (200t)^2 dt + \int_{0.075}^{0.1} (60 - 600t)^2 dt \\ &= 5.625 + 1.875 = 7.5 \end{aligned}$$

$$\therefore I_{rms} = \sqrt{\frac{7.5}{0.1}} = \sqrt{75} = 8.66 \text{ A(rms)}$$

10.10

③

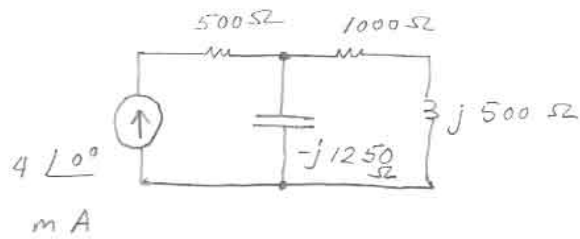

$$\bar{Z}_{eq} = 500 + (-j1250) \parallel (1000 + j500)$$

$$= 500 + \frac{(-j1250)(1000 + j500)}{-j1250 + (1000 + j500)}$$

$$= 500 + \frac{(1250 \angle -90^\circ)(1118.04 \angle 26.57^\circ)}{1250 \angle -36.87^\circ}$$

$$= 500 + 1118.04 \angle -26.56^\circ = 500 + (1000 - j500)$$

$$= 1500 - j500 \Omega$$

Since only the resistive part of the impedance absorbs average power, then the average power absorbed by the load:


$$P_L = P_R = \frac{1}{2} I^2 R = \frac{1}{2} (0.004)^2 (1500) = 12 \text{ mW}$$

$\therefore$  The source delivers 12 mW to the load.

10.15

(4)

a)

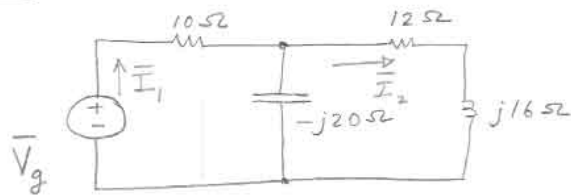

$$\bar{V}_g = 170 \angle 0^\circ \text{ V (rms)}$$

$$\text{KVL} \Rightarrow -170 + 10\bar{I}_1 + (-j20)(\bar{I}_1 - \bar{I}_2) = 0 \Rightarrow$$

$$(10 - j20)\bar{I}_1 + j20\bar{I}_2 = 170 \quad (1)$$

$$\text{KVL} \Rightarrow -j20(\bar{I}_2 - \bar{I}_1) + (12 + j16)\bar{I}_2 = 0$$

$$j20\bar{I}_1 + (12 - j4)\bar{I}_2 = 0 \quad (2)$$

$$\text{solving } (1) \text{ \& } (2) \Rightarrow \bar{I}_1 = (4 + j) \text{ A}$$

$$\bar{I}_2 = (3.5 - j3.5) \text{ A}$$

$$\bar{S}_g = -\bar{V}_g \bar{I}_1^* = (-170 \angle 0^\circ)(4 - j)$$

$$= -680 + j170 \text{ VA}$$

$$b) P_g = -680 \text{ W (del.)}$$

$$c) Q_g = 170 \text{ VAR (abs.)}$$

$$d) P_{10\Omega} = \bar{I}_1^2 10 = 10(17) = 170 \text{ W}$$

$$Q_{10\Omega} = 0$$

$$P_{12\Omega} = 12 \bar{I}_2^2 = 12(3.5^2 + 5.5^2) = 510 \text{ W}$$

(5)

$$Q_{12\Omega} = 0$$

$$P_{-j20\Omega} = 0, \quad Q_{-j20\Omega} = -20 |\bar{I}_1 - \bar{I}_2|^2 = -20(0.5^2 + 6.5^2) \\ = -850 \text{ VAR}$$

$$P_{j16\Omega} = 0, \quad Q_{j16\Omega} = 16 \bar{I}_2^2 = 16(3.5^2 + 5.5^2) = 680 \text{ VAR}$$

$$e) \quad \sum P_{\text{del.}} = 680 \text{ W}$$


$$\sum P_{\text{abs}} = 170 + 510 = 680 \text{ W}$$

$$f) \quad \sum Q_{\text{del.}} = 850 \text{ VAR}$$

$$\sum Q_{\text{abs}} = 170 + 680 = 850 \text{ VAR}$$

10.17 a)

⑥

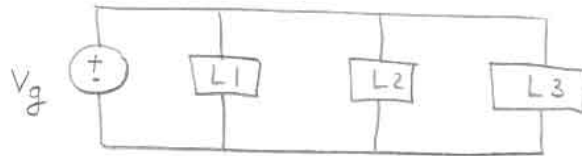

$$\bar{Z}_1 = 240 + j70 \Omega = 250 \angle 16.26^\circ$$

$$\therefore Pf_1 = \cos \theta_1 = \cos 16.26^\circ = 0.96 \text{ (lagging)}$$

$$\therefore rf_1 = \sin \theta_1 = \sin 16.26^\circ = +0.28$$

$$\bar{Z}_2 = 160 - j120 \Omega = 200 \angle -36.87^\circ$$

$$Pf_2 = \cos(-36.87^\circ) = 0.8 \text{ (leading)}$$

$$rf_2 = \sin(-36.87^\circ) = -0.6$$

$$\bar{Z}_3 = 30 - j40 \Omega = 50 \angle -53.13^\circ \Omega$$

$$Pf_3 = \cos(-53.13^\circ) = 0.6 \text{ (leading)}$$

$$rf_3 = \sin(-53.13^\circ) = -0.8$$

$$\begin{aligned} \text{b) } \bar{Z}_{eq} &= \frac{1}{Y_{eq}}, \quad Y_{eq} = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 \\ &= \frac{1}{250 \angle 16.26^\circ} + \frac{1}{200 \angle -36.87^\circ} + \\ &\quad \frac{1}{50 \angle -53.13^\circ} \end{aligned}$$

$$= 0.004 \angle -16.26^\circ + 0.005 \angle 36.87^\circ + 0.02 \angle 53.13^\circ \quad \textcircled{7}$$

$$= 0.01984 + j0.01788 \quad (S)$$

$$\therefore \bar{Z}_{eq} = \frac{1}{0.01984 + j0.01788} = \frac{1}{0.02671 \angle 42.025^\circ}$$


$$= 37.44 \angle -42.025^\circ \quad \Omega$$

$$\therefore Pf = \cos 42.025^\circ = 0.743 \text{ (leading).}$$

$$\therefore rf = \sin(-42.025^\circ) = -0.669$$

10.18 a)

$$\bar{S}_1 = (16 + j18) \text{ KVA}$$

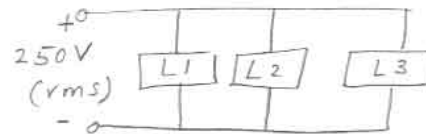

$$\theta_2 = -\cos^{-1}(0.6) = -53.13^\circ$$

$$S_2 = |\bar{S}_2| = 10 \text{ KVAR}$$

$$\frac{P_2}{S_2} = \cos \theta_2 \Rightarrow P_2 = S_2 \cos(-53.13^\circ) = S_2 (Pf_2)$$

$$= 10(0.6) = 6 \text{ KW}$$

$$\frac{Q_2}{S_2} = \sin \theta_2 \Rightarrow Q_2 = S_2 \sin(-53.13^\circ) = S_2 (rf_2)$$

$$= 10(-0.8) = -8 \text{ KVAR}$$

$$\therefore \bar{S}_2 = (6 - j8) \text{ KVA}$$

$$\bar{S}_3 = 8 \text{ KW}, \text{ since } Pf_3 = 1 \Rightarrow Q_3 = 0.$$

$$\begin{aligned}\bar{S}_{\text{tot}} &= \bar{S}_1 + \bar{S}_2 + \bar{S}_3 = (6 + j18) + (6 - j8) + 8 \\ &= (30 + j10) \text{ KVA}\end{aligned}$$

(2)

$$\bar{S}_{\text{tot}} = \bar{V} \bar{I}^* \Rightarrow (30 + j10) \text{ K} = 250 \bar{I}^*$$

$$\bar{I}^* = \frac{30000 + j10000}{250} = (120 + j40) \text{ A (rms)}$$

$$\therefore \bar{I} = (120 - j40) \text{ A (rms)}$$

$$\therefore \bar{Z}_{\text{eq}} = \frac{\bar{V}}{\bar{I}} = \frac{250 \angle 0^\circ \text{ V (rms)}}{(120 - j40) \text{ A (rms)}}$$

$$= 1.98 \angle 18.43^\circ \Omega$$

$$b) \text{ pf} = \cos(18.43^\circ) = 0.949 \text{ (lagging).}$$