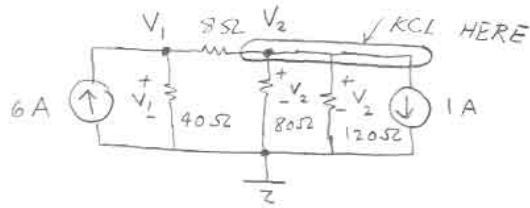


4.9



Node 1 \Rightarrow

$$-6 + \frac{V_1}{40} + \frac{V_1 - V_2}{8} = 0$$

$$-240 + V_1 + 5V_1 - 5V_2 = 0 \Rightarrow 6V_1 - 5V_2 = 240 \quad (1)$$

Node 2 \Rightarrow

$$\frac{V_2 - V_1}{8} + \frac{V_2}{80} + \frac{V_2}{120} + 1 = 0$$

$$30V_2 - 30V_1 + 3V_2 + 2V_2 + 240 = 0 \Rightarrow -30V_1 + 35V_2 = -240 \quad (2)$$

Solving $\Rightarrow V_1 = 120V \neq V_2 = 96V$

4.10

a) Node 1 \Rightarrow

$$\frac{V_1 - 44}{4} + \frac{V_1}{6} + \frac{V_1 - V_2}{1} = 0$$

$$3V_1 - 132 + 2V_1 + 12V_1 - 12V_2 = 0$$

$$17V_1 - 12V_2 = 132 \quad (1)$$

Node 2 $\Rightarrow V_2 - V_1 + \frac{V_2}{3} + \frac{V_2 - (-2)}{2} = 0$


$$6V_2 - 6V_1 + 2V_2 + 3V_2 + 6 = 0$$

$$-6V_1 + 11V_2 = -6 \quad (2)$$

Solving $\Rightarrow V_1 = 12V \neq V_2 = 6V$

$$i_a = \frac{44 - V_1}{4} = \frac{44 - 12}{4} = 8A, \quad i_b = \frac{V_1}{6} = 2A, \quad i_c = \frac{12 - 6}{1} = 6A$$
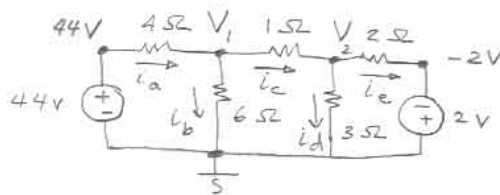
$$i_d = \frac{6}{3} = 2A, \quad i_e = \frac{6 - (-2)}{2} = 4A$$



4.10 b)

2/5

$$P_{44V} = -8 \times 44 = -352W, \quad P_{2V} = -4 \times 2 = -8W$$


$$\therefore P_{\text{developed}} = 352 + 8 = 360W$$

4.17

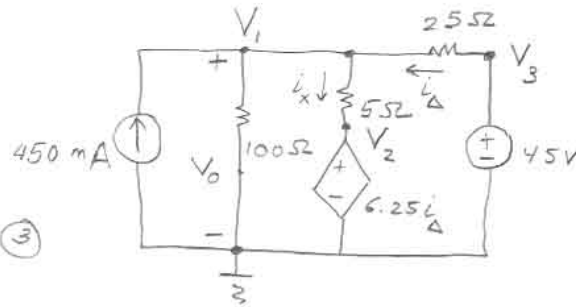a) $V_3 = 45V$ ①

$$V_2 = 6.25i_{\Delta} \quad \text{②}$$

$$i_{\Delta} = \frac{V_3 - V_1}{25} = \frac{45 - V_1}{25} \quad \text{③}$$



substitute ③ into ② \Rightarrow

$$V_2 = 6.25 \left(\frac{45 - V_1}{25} \right) = \frac{1}{4} (45 - V_1) \Rightarrow$$

$$4V_2 = 45 - V_1 \Rightarrow V_1 + 4V_2 = 45 \quad \text{④}$$

$$\text{Node 1} \Rightarrow -450 \times 10^{-3} + \frac{V_1}{100} + \frac{V_1 - V_2}{5} + \frac{V_1 - V_3}{25} = 0$$

$$-45 + V_1 + 20V_1 - 20V_2 + 4V_1 - 4V_3 = 0$$

$$25V_1 - 20V_2 - 45 - 4(45) = 0$$

$$25V_1 - 20V_2 = 225 \quad \text{⑤}$$

$$\text{solving ④ \& ⑤} \Rightarrow V_1 = V_0 = 15V$$

b) $i_{\Delta} = \frac{V_3 - V_1}{25} = \frac{45 - 15}{25} = \frac{30}{25} = 1.2A$

$$6.25i_{\Delta} = 6.25(1.2) = 7.5V = V_2 \quad \& \quad i_x = \frac{V_1 - V_2}{5} = \frac{15 - 7.5}{5} = 1.5A$$

$$\therefore P_{6.25i_{\Delta}} = i_x V_2 = 1.5(7.5) = 11.25W$$

4.17 c)


3/5

$$P_{450mA} = -450 \times 10^{-3} (15) = -6.75W \text{ (developed)}$$

$$P_{45V} = -1.2 \times 45 = -54W \text{ (developed)}$$

\therefore Total power developed by the independent sources is $6.75 + 54 = 60.75W$

4.2.2

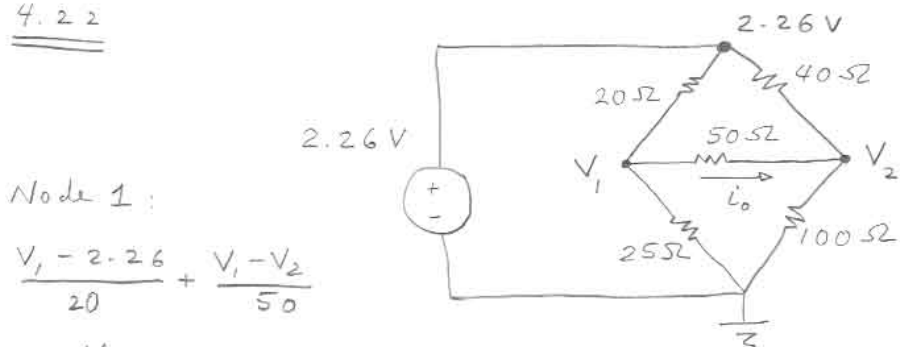

Node 1:

$$\frac{V_1 - 2.26}{20} + \frac{V_1 - V_2}{50}$$

$$+ \frac{V_1}{25} = 0 \Rightarrow$$

$$5V_1 - 11.3 + 2V_1 - 2V_2 + 4V_1 = 0$$

$$11V_1 - 2V_2 = 11.3 \quad (1)$$

$$\text{Node 2} \Rightarrow \frac{V_2 - 2.26}{40} + \frac{V_2 - V_1}{50} + \frac{V_2}{100} = 0$$

$$5V_2 - 11.3 + 4V_2 - 4V_1 + 2V_2 = 0$$

$$-4V_1 + 11V_2 = 11.3 \quad (2)$$

$$\text{Solving} \Rightarrow V_1 = 1.3V \quad \& \quad V_2 = 1.5V$$

$$\therefore i_o = \frac{V_1 - V_2}{50} = \frac{1.3 - 1.5}{50} = -4mA$$

4.25

4/3

Node 1 \Rightarrow

$$7 + \frac{V_1}{3} + \frac{V_1 - V_2}{1} = 0$$

$$4V_1 - 3V_2 = -21 \quad (1)$$

Node 2 \Rightarrow

$$\frac{V_2 - 4}{2} + \frac{V_2 - V_1}{1} - 2V_x = 0 \quad \text{and} \quad V_x = V_2 - 4 \Rightarrow$$


$$\frac{V_2 - 4}{2} + \frac{V_2 - V_1}{1} - 2(V_2 - 4) = 0$$

$$V_2 - 4 + 2V_2 - 2V_1 - 4V_2 + 16 = 0$$

$$-2V_1 - V_2 = -12 \quad (2)$$

solving $\Rightarrow V_1 = 1.5 \text{ V} \neq V_2 = 9 \text{ V}$

$$\therefore V_o = V_1 = 1.5 \text{ V}$$

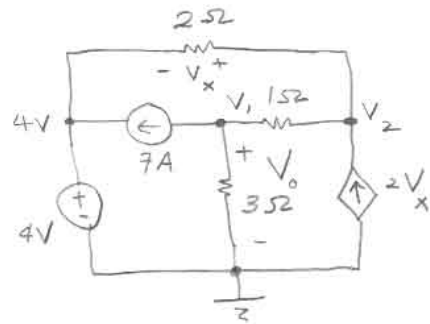


4.27

$$V_1 - V_2 = 4V_\Delta \quad (1)$$

$$V_\Delta = V_2 \quad (2)$$

Substitute (2) into (1) $\Rightarrow V_1 - V_2 = 4V_2 \Rightarrow$

$$V_1 - 5V_2 = 0 \quad (3)$$

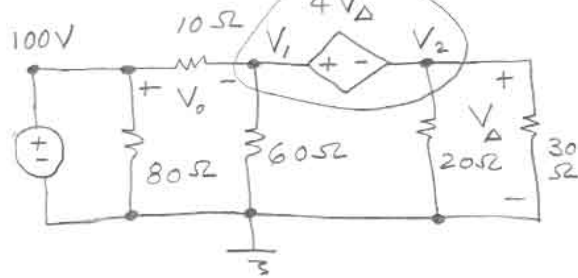

KCL at the supernode \rightarrow

5/5

$$\frac{V_1 - 100}{10} + \frac{V_1}{60} + \frac{V_2}{20} + \frac{V_2}{30} = 0$$

$$6V_1 - 600 + V_1 + 3V_2 + 2V_2 = 0$$

$$7V_1 + 5V_2 = 600 \quad (4)$$

solving (3) & (4) \Rightarrow

$$V_1 = 75 \quad \neq \quad V_2 = 15V$$

$$\therefore V_0 = 100 - V_1 = 100 - 75 = 25V$$