

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

FIRST SEMESTER 2007/2008

EE 201 MAJOR EXAM II

DATE: TUESDAY 11-12-2007

TIME: 6:30-8:00 PM

Locations:

Dr. Samir Abdul-Jauwad (Section 04): Building **24**, Room **128**.

Dr. Abdallah Al-Ahmari (Sections 02 & 05): Building **24**, Room **120**.

Dr. Adel Balghonaim (Section 07): Building **24**, Room **129**.

Dr. Husain Masoudi (Sections 06 & 08): Building **14**, Room **108**.

Dr. Husain Al-Jamid (Section 01): Building **14**, Room **108**.

Student's Name:.....

Student's I.D. Number:.....



Section Number:

	Maximum Score	Score
Problem 1 (a)	10	
Problem 1 (b)	10	
Problem 2 (a)	13	
Problem 2 (b)	7	
Problem 3	20	
Total	60	

Problem 1 (a) [10 pts]

i) Find the output voltage V_o in the Op Amp circuit shown in figure 1.

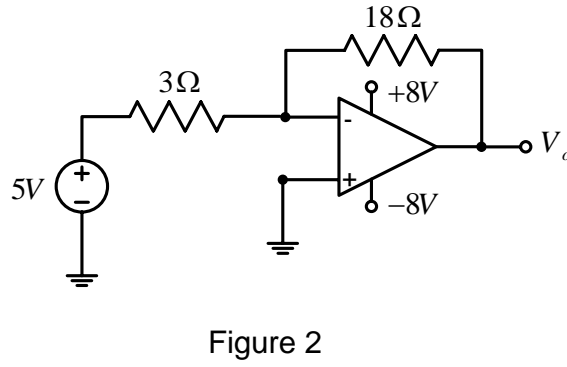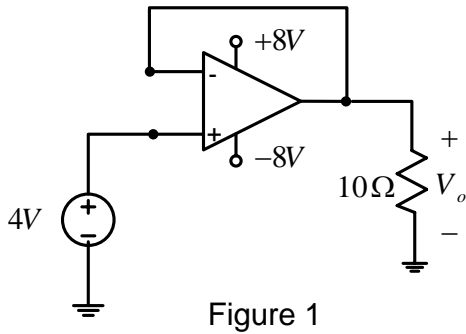ii) Find the output voltage V_o in the Op Amp circuit shown in figure 2.




Answers:

i) $V_o =$

ii) $V_o =$

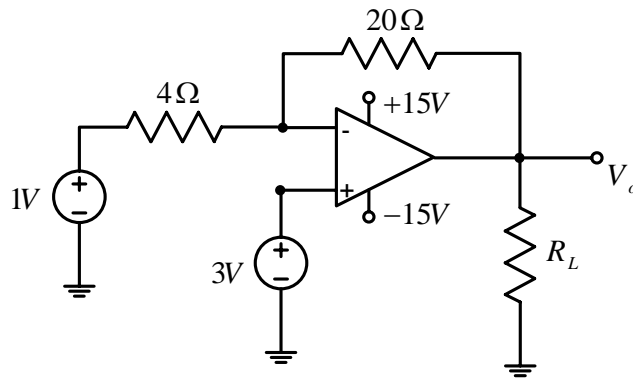Problem 1 (b) [10 pts]

In the Op Amp circuit shown, the load resistor R_L and the 4Ω resistor absorb *equal* powers. Calculate the value of the load resistor R_L .




Answer:

$R_L =$

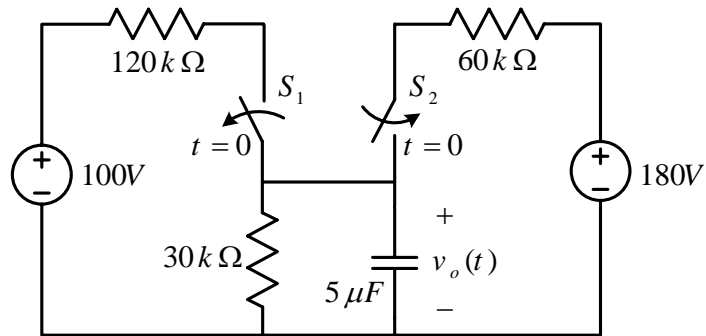Problem 2 (a) [13 pts]

In the circuit shown, switch S_1 has been closed and switch S_2 has been open for a long time. At $t = 0$, switch S_1 is opened and switch S_2 is closed suddenly.

- i)** Find the voltage $v_o(t)$ for $t < 0$. **ii)** Find the voltage $v_o(t)$ for $t \geq 0$. **iii)** Plot $v_o(t)$ for all t .



ANSWERS

i) For $t < 0$, $v_o(t) =$

ii) For $t \geq 0$, $v_o(t) =$



iii) Plot of $v_o(t)$

Problem 2 (b) [7 pts]

In the given circuit, the variation of the current $i_s(t)$ with time is shown graphically.

i) Find the time *instants* at which the energy stored in the 5 H inductor equals 40 J.

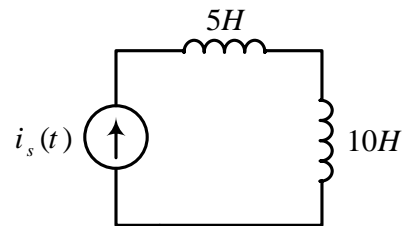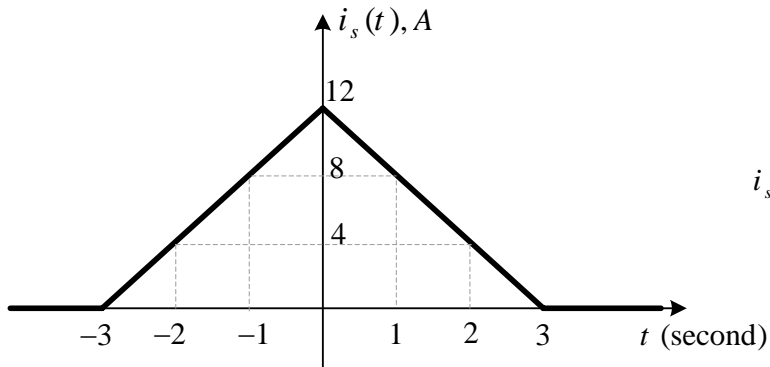ii) Calculate the power in the 10 H inductor at $t = 1$ second. Is this power actually absorbed or actually delivered by the 10 H inductor?



Answers:

i) Time instants in second =

ii) $P_{10H}(1) =$


Actually absorbed

Actually delivered

Problem 3 [20 pts]

As shown below, the load resistor R_L is connected to the circuit at terminals a and b .

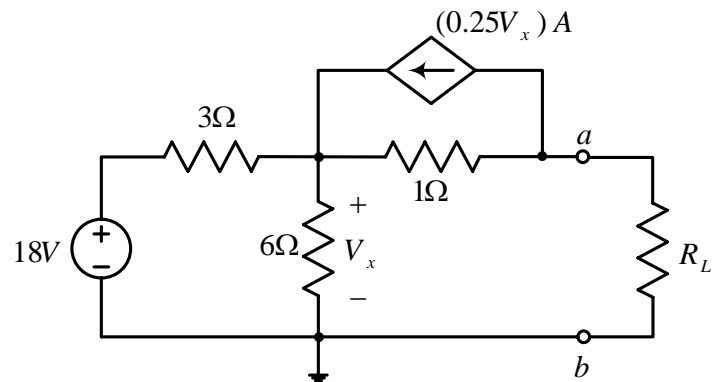- a) Find the value of R_L that absorbs maximum power from the circuit.
- b) Calculate the open circuit voltage between the terminals a and b .
- c) Calculate the maximum power absorbed by R_L .



<p>Answers:</p> <p>a) $R_L =$</p> <p>b) $V_{oc} =$</p> <p>c) $P_{max} =$</p>
--