

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE 201 (071)
Quiz # 1

Name: _____
ID#: _____
Section No: _____

- For the circuit below find the following:
- a) The power dissipated by the 20 Ω resistor.
 - b) The power dissipated by the 5 Ω resistor.