

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE 201 (071)
Quiz # 2

Name: _____
ID#: _____
Section No: _____

For the following circuit:

- a) Use the Node-voltage method to derive the system of equations and simplify them without solution.
- b) Find the voltage v_o as function of the node voltages.

