

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE 201 (071)
Quiz # 4

Name: _____
ID#: _____
Section No: _____

For the following circuit:

- a) Sketch the current i_x .
- b) Sketch the current i_y .

(Show all of your solution steps)

