

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE 201 (071)
Quiz # 5

Name: _____
ID#: _____
Section No: _____

For the following circuit, sketch the current $i_o(t)$.

(Show all of your solution steps)

