

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE 201 (071)
Quiz # 6

Name: _____
ID#: _____
Section No: _____

Find the Thevenin equivalent circuit with respect to the terminals a,b for the following circuit.

