

$$P 11.24 \quad [a] \quad P_{OUT} = 746 \times 200 = 149,200 \text{ W}$$

$$P_{IN} = 149,200 / (0.96) = 155,416.67 \text{ W}$$

$$\sqrt{3} V_L I_L \cos \theta = 155,416.67$$

$$I_L = \frac{155,416.67}{\sqrt{3}(208)(0.92)} = 468.91 \text{ A}$$

$$66,207.79 \text{ VAR}$$

$$[b] \quad Q = \sqrt{3} V_L I_L \sin \phi = \sqrt{3}(208)(468.91)(0.39) = 66,207.79 \text{ VAR}$$

P 11.27 [a]  $S_1 = 72 - j21 \text{ kVA}$


$S_2 = 120 + j90 \text{ kVA}$

$S_3 = 168 + j36 \text{ kVA}$

$S_T = S_1 + S_2 + S_3 = 360 + j105 \text{ kVA}$

$S_T/\phi = 120 + j35 \text{ kVA}$

Single phase equivalent circuit

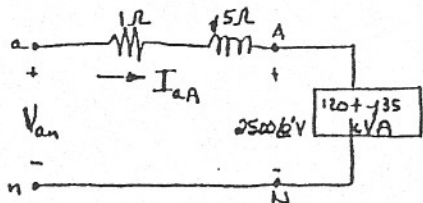

$\therefore I_{aA} = \frac{120,000 + j35,000}{2500} = 48 + j14$

$\therefore I_{aA} = 48 - j14 \text{ A} = 50 \angle -16.26^\circ \text{ A}$

$V_{an} = 2500 + (1 + j5)(48 - j14) = 2618 + j226$   
 $= 2627.74 \angle 4.93^\circ \text{ V}$


$\therefore |V_{ab}| = \sqrt{3}(2627.74) = 4534.51 \text{ V}$

[b]  $P_L/\phi = 120 \text{ kW}$

$P_S/\phi = 120,000 + |I_{aA}|^2(1) = 122,500 \text{ W} = 122.5 \text{ kW}$

$\eta = \left(\frac{120}{122.5}\right) 100 = 97.96\%$

P 11.28 [a]

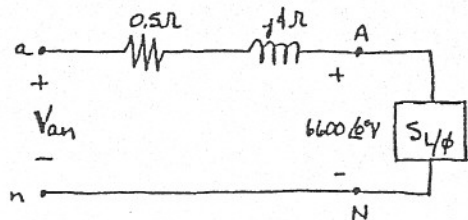

$S_{L/\phi} = \frac{1}{3} \left[ 1188 + j \frac{1188}{0.6} (0.8) \right] 10^3 = 396,000 + j528,000 \text{ VA}$


$I_{aA} = \frac{396,000 + j528,000}{6600} = 60 + j80 \text{ A}$

$I_{nA} = 60 - j80 \text{ A}$

$V_{an} = 6600 + (60 - j80)(0.5 + j4)$   
 $= 6950 + j200 = 6952.88 \angle 1.65^\circ \text{ V}$

$|V_{ab}| = \sqrt{3}(6952.88) = 12,042.74 \text{ V}$

[b]

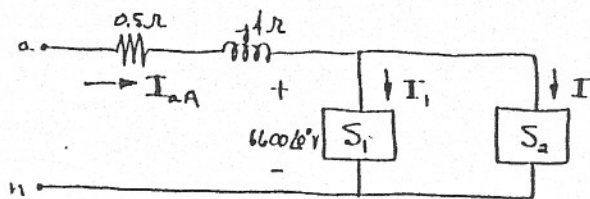

$I_1 = 60 - j80 \text{ A}$  (from part [a])

$S_2 = 0 - j \frac{1}{3} (1920) \times 10^3 = -j640,000 \text{ VAR}$

$I_2 = \frac{-j640,000}{6600} = -j96.97 \text{ A}$

$\therefore I_2 = j96.97 \text{ A}$

$I_{aA} = 60 - j80 + j96.97 = 60 + j16.97 \text{ A}$

$V_{an} = 6600 + (60 + j20)(0.5 + j4)$   
 $= 6550 + j250 = 6554.77 \angle 2.19^\circ \text{ V}$

$|V_{ab}| = \sqrt{3}(6554.77) = 11,353.19 \text{ V}$

[c]  $I_{aA} = 100 \text{ A}$

$P_{\text{loss}/\phi} = (100)^2(0.5) = 5000 \text{ W}$

$P_{T/\phi} = 396,000 + 5000 = 401 \text{ kW}$

$\% \eta = \frac{396}{401}(100) = 98.75\%$

[d]  $|I_{aA}| = \sqrt{4000} \text{ A} = 62.35$

$P_{T/\phi} = (4000)(0.5) = 2000 \text{ W} = 1944$

$\% \eta = \frac{396}{398}(100) = 99.50\% = 99.51\%$

397.974

$$[e] \quad Z_{\text{cap}/Y} = -j \frac{6600}{100} = -j66 \Omega = -j69 \Omega$$

$$Z_{\text{cap}/\Delta} = 3Z_{\text{cap}/Y} = -j192 \Omega$$

$$Z_{\text{cap}\Delta} = -j264$$

for  $\Delta$  connected capacitors.

$$\therefore \frac{1}{\omega C} = 192; \quad C = \frac{1}{(192)(120\pi)} = 13.4 \mu\text{F}$$

$$P 11.38 \quad \tan \phi = \frac{\sqrt{3}(W_2 - W_1)}{W_1 + W_2} = \frac{873,290.66}{732,777.88} = 1.1918$$

$$\therefore \phi = 50^\circ ;$$

$$\therefore 7600\sqrt{3}|I_L| \cos 80^\circ = 114,291.64$$

$$|I_L| = 50 \text{ A}$$

$$|Z| = \frac{7600}{50} = 152 \Omega \quad \therefore Z = 152/\underline{50}^\circ \Omega$$