
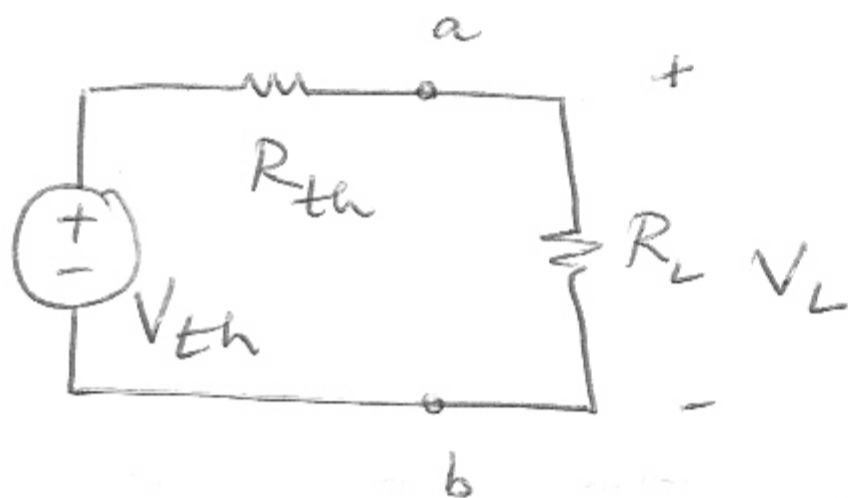
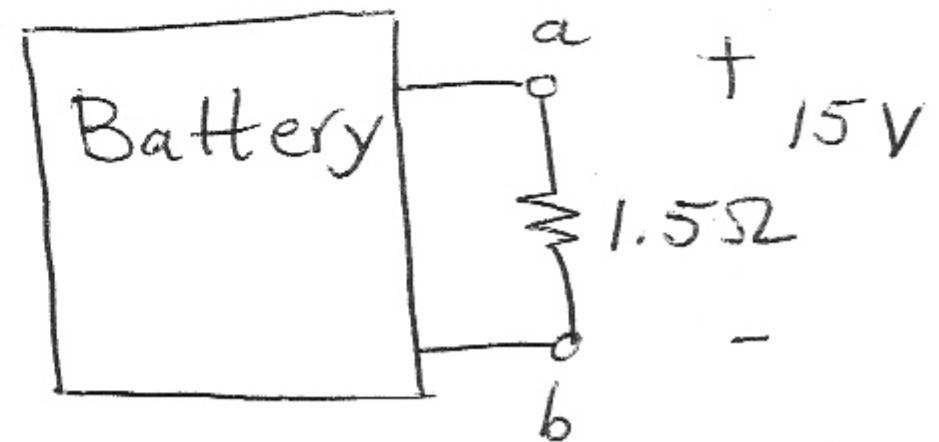


Name:

I.D. Number:

KEY

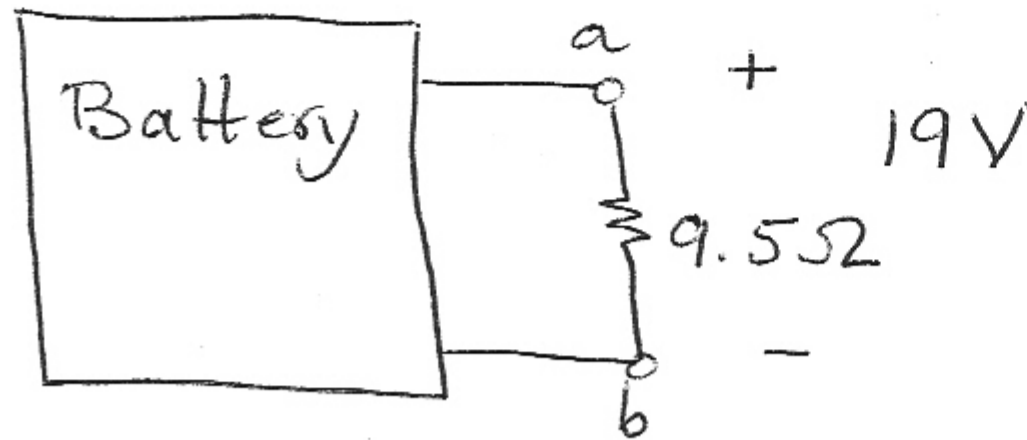Consider a battery with an unknown Thevenin equivalent circuit. When a  $9.5\Omega$  load resistor is connected to the battery, the voltage developed across the load equals 19 V. When a  $1.5\Omega$  load resistor is connected to the same battery, the voltage developed across the load equals 15 V. Find Thevenin's equivalent circuit of the battery.



$$V_L = \frac{R_L}{R_L + R_{th}} V_{th}$$

$$\therefore 19 = \frac{9.5}{R_{th} + 9.5} V_{th} \quad (1)$$

$$15 = \frac{1.5}{R_{th} + 1.5} V_{th} \quad (2)$$

$$\text{solving } (1) \text{ \& } (2) \Rightarrow V_{th} = 20V$$

$$R_{th} = 0.5\Omega$$