

EE 201 Assignment # 4

Dr. H. M. Masoudi

Use Multisim software to simulate the Plot of v for all time in the circuit shown.

Before solving this problem, please read and apply the illustration example given for assignment 4 and 5. For clear presentation use 100 ms/Div for time scale and 10 V/Div for voltage scale in the oscilloscope window. Start the simulation and then hit the space bar to change the position of the switch and record only 1 s of simulation time.

