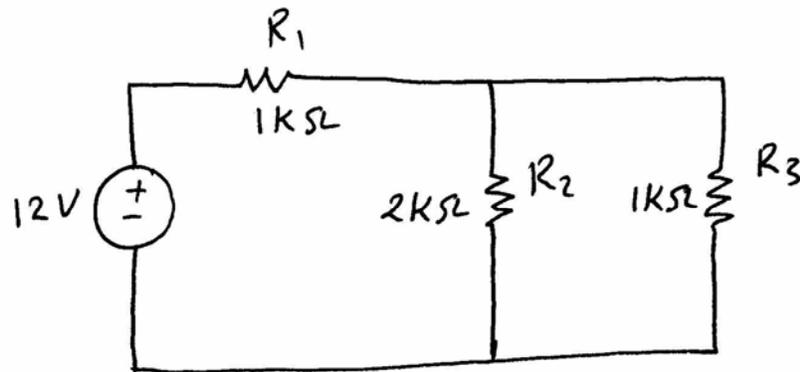


EE 201 Assignment - 1

H. M. Masoudi, Ph.D.

Use Multisim Software to calculate the current in R_1 and the voltage across R_3 in the circuit shown below.



To submit assignments always use the guidelines given in the guidelines document.