



ELECTRONICS I

First Major Exam

EE 203 – Winter 2008 (072)

Wednesday, March 19th, 2008

18H00 – 19H30 (1 hour – 30 minutes)

Name _____

Student ID _____

Section _____ 4 _____


Examiner – Dr. Alaa El-Din Hussein

- This exam contains **four questions** and is composed of 5 pages including this cover page. Partial point distribution is indicated between brackets. Please pace yourself accordingly.
- This is a **CLOSED book** examination.
- Make sure to **state all assumptions** you find necessary to complete your answer.
- Show **all** your work. Partial credit will be given. If you think you need something that you can't remember, write down what you need and what you'd do if you remembered it.

Question #	Question 1	Question 2	Question 3	Question 4	Total
Mark					
Total Mark	10	10	10	10	40

Question 2:


Find the Q-points (I_D , V_D) for all the diodes in the shown circuit using the constant voltage drop model with $V_D = 0.7V$. For the zener diode $V_Z = 4.7V$ and $r_z = 0 \Omega$.

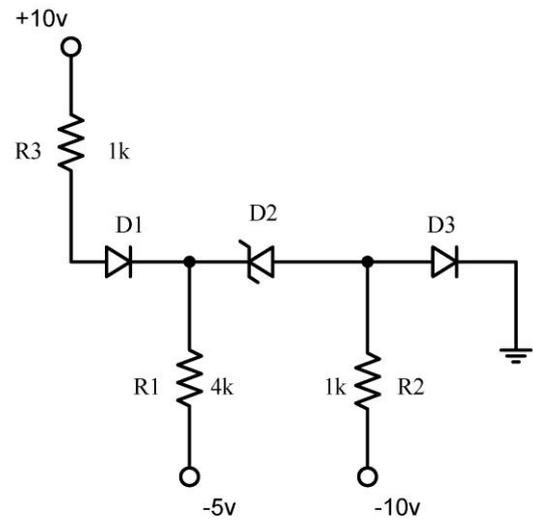[10 Marks]

Question 3:**[10 Marks]**

It is required to use the shown rectifier circuit below to design a DC power supply that provides an average DC output voltage of 10V on which a maximum of $\pm 0.6V$ ripple is allowed. The available diodes have 0.7V drops when conducting.

- What is the rectifier type (Full/Half) wave **[1 Mark]**
- Specify the rms voltage that must appear across the transformer secondary (v_s). **[3 Marks]**
- Specify the value of N for the shown transformer **[1 Mark]**
- Find the required value of the filter capacitor. **[3 Marks]**
- Find the maximum reverse voltage that will appear across the diode **[2 Marks]**

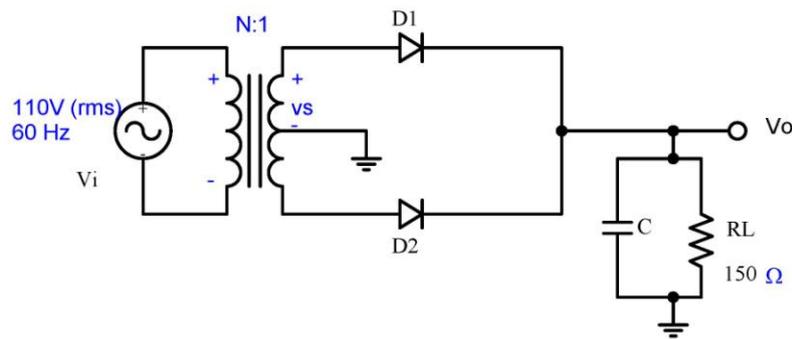

Question 3:**[10 Marks]**

For the shown transistor circuit assume that the threshold voltage $V_{TN} = 1V$, and the transconductance parameter $k_n = 1 \text{ mA/V}^2$.

- Analyze the circuit to find the transistor operating point (I_D , V_{DS}). **[5 Marks]**
- What is the transistor region of operation **[1 Marks]**
- If R_{G2} is removed (open circuited), what will be the effect on the transistor region of operation?, calculate the new operating point **[4 Marks]**

