



<i>Name:</i>		
<i>Student ID:</i>	<b>Section: 4</b>	<b>Quiz: 1</b>

For the shown circuit calculate  $I$  and  $V_a$  assuming ideal diodes? What are the status of each diode (ON, or OFF). Check your assumptions.

